

# **Lab 1: Device Characterization and Biasing Circuits**

Professor: Dr. Chih-Hung (James) Chen

Name: Erion Keka

Student Number: 400435050

Submission Date: 2024-09-22

**Q1. (7 Points)** Based on the simulated data in Steps 1.2-1.4, use the bias condition giving the closest  $I_C$  value to the desired collector current, find out

- (1) What are the simulated  $V_{BEon}$  in volts and the base current  $I_B$  in  $\mu A$ ?

$$V_{BEon} = 0.621 \text{ V and } I_B = 8.79 \mu A$$

- (2) What is the  $\beta = I_C/I_B$  value at this  $I_C$ ?

$$\beta = 117$$

- (3) What is the early voltage  $|V_A|$  in volts?

$$|V_A| = 935 \text{ V}$$

- (4) What is the output resistance  $r_o$  in  $k\Omega$ ?

$$r_o = 912 \text{ k}\Omega$$

- (5) What is the transconductance  $g_m$  in  $mS$ ?

$$g_m = 41 \text{ mS}$$

- (6) What is the input resistance  $r_\pi$  in  $k\Omega$ ?

$$r_\pi = 2.845 \text{ k}\Omega$$

**Q2. (8 Points)** Based on the measured data in Step 1.8, use the same bias condition found in Q1 (or the first reliable data if that bias condition is an outlier), find out

- (1) How much is the measured collector current  $I_C$  in  $mA$ ?

$$I_C = 1.22 \text{ mA}$$

- (2) What are the measured  $V_{BEon}$  in volts and the base current  $I_B$  in  $\mu A$ ?

$$V_{BEon} = 0.64742 \text{ V and } I_B = 3.52 \mu A$$

- (3) What is the  $\beta = I_C/I_B$  value at this  $I_C$ ?

$$\beta = 346$$

- (4) What is the early voltage  $|V_A|$  in volts?

$$|V_A| = 260 \text{ V}$$

- (5) What is the output resistance  $r_o$  in  $k\Omega$ ?

$$r_o = 214 \text{ k}\Omega$$

- (6) What is the transconductance  $g_m$  in  $mS$ ?

$$g_m = 48.6 \text{ mS}$$

- (7) What is the input resistance  $r_\pi$  in  $k\Omega$ ?

$$r_\pi = 7.112 \text{ k}\Omega$$


**Q3. (7 Points)** Based on the simulated data in Steps 2.2-2.4, use the bias condition giving the closest  $I_C$  value to the desired collector current, find out.

- (1) What are the simulated  $V_{E_{on}}$  in volts and the base current  $I_B$  in  $\mu A$ ?  
 $V_{E_{on}} = 0.66 \text{ V}$  and  $I_B = 8.40 \mu A$
- (2) What is the  $\beta = I_C/I_B$  value at this  $I_C$ ?  
 $\beta = 126$
- (3) What is the early voltage  $|V_A|$  in volts?  
 $|V_A| = 140 \text{ V}$
- (4) What is the output resistance  $r_o$  in  $k\Omega$ ?  
 $r_o = 131 \text{ k}\Omega$
- (5) What is the transconductance  $g_m$  in  $mS$ ?  
 $g_m = 42.5 \text{ mS}$
- (6) What is the input resistance  $r_\pi$  in  $k\Omega$ ?  
 $r_\pi = 2.976 \text{ k}\Omega$

**Q4. (8 Points)** Based on the measured data in Step 2.8, use the same bias condition found in Q3 (or the first reliable data if that bias condition is an outlier), find out

- (1) How much is the measured collector current  $I_C$  in  $mA$ ?  
 $I_C = 1.76 \text{ mA}$
- (2) What are the measured  $V_{E_{on}}$  in volts and the base current  $I_B$  in  $\mu A$ ?  
 $V_{E_{on}} = 0.685 \text{ V}$  and  $I_B = 8.15 \mu A$
- (3) What is the  $\beta = I_C/I_B$  value at this  $I_C$ ?  
 $\beta = 216$
- (4) What is the early voltage  $|V_A|$  in volts?  
 $|V_A| = 32 \text{ V}$
- (5) What is the output resistance  $r_o$  in  $k\Omega$ ?  
 $r_o = 18.3 \text{ k}\Omega$
- (6) What is the transconductance  $g_m$  in  $mS$ ?  
 $g_m = 70.3 \text{ mS}$
- (7) What is the input resistance  $r_\pi$  in  $k\Omega$ ?  
 $r_\pi = 3.069 \text{ k}\Omega$

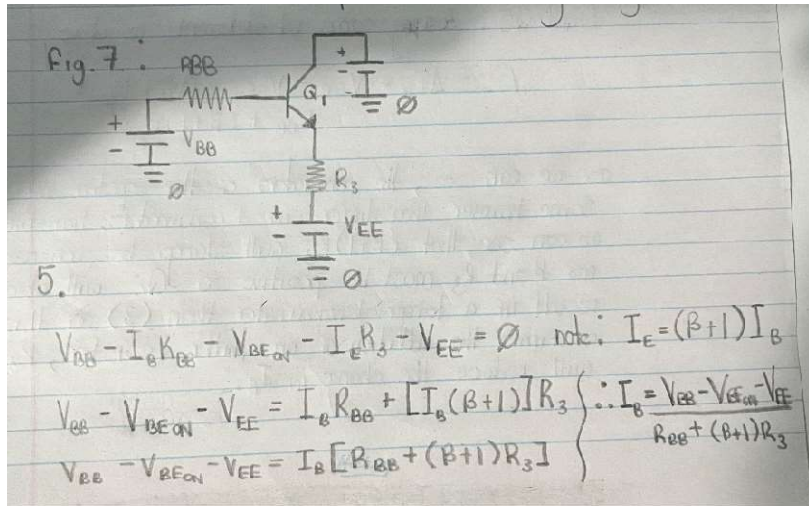**Q5. (10 Points)** Express the base current  $I_B$  as a function of  $V_{BB}$ ,  $R_{BB}$ ,  $V_{BEon}$ ,  $R_3$ ,  $V_{EE}$ , and  $\beta$ .



**Q6. (10 Points)** Comparing the IB expressions obtained in Q5 and in (3), what is the difference between these two equations? For a change  $\Delta V_{EE}$  in the power supply VEE, derive equations for the resulting change in the base current  $\Delta I_B$  using the IB expressions obtained in Q5 and in (3). Show that the emitter resistor  $R_3$  reduces the change in the base current  $\Delta I_B$  as a result of the change  $\Delta V_{EE}$  in the power supply VEE.

6.  $I_B$  expression (3):  $I_B = \frac{V_{BB} - (V_{BE} + V_{BEQ1})}{R_{BB}}$

$I_B$  expression Q5:  $I_B = \frac{V_{BB} - V_{BEQ1} - V_{EE}}{R_{BB} + (\beta + 1)R_3}$

From first glance, we notice that these two equations differ in (3) lacking  $R_3$ . Equation (3) lacks  $R_3$  as we have taken it to be  $\emptyset$  based on  $V_{BEQ1}$  as mentioned in the lab manual. The presence of  $R_3$  in Q5 is due to not taking it to be  $\emptyset$  thus, we get  $(\beta + 1)R_3$  in Q5 equation.

derived equation (3): let  $\Delta V_{CE} = V_{EE} + \Delta V_{EE}$  and  $\Delta I_B = I_B + \Delta I_B$

$$\Delta I_B = \frac{V_{BB} - [(V_{EE} + \Delta V_{EE}) + V_{BEQ1}]}{R_{BB}}$$

derived Q5: using same let statements as above

$$\Delta I_B = \frac{V_{BB} - V_{BEQ1} - (V_{EE} + \Delta V_{EE})}{R_{BB} + (\beta + 1)R_3}$$

as we can see, the numerators of the equations are same however they differ in denominators. From this, we can see that  $(\beta + 1)R_3$  will always be non-negative as  $\beta$  and  $R_3$  must be positive so Q5 will always result in a larger denominator than (3) so this confirms the addition of an emitter resistor,  $R_3$  will reduce the change in  $I_B$ .

**Q7. (10 Points)** Inserting the feedback  $R_3$  at the emitter of the BJT improves the stabilization of the Q-point at the cost of increased  $V_{o,min}$ . What is the  $V_{o,min}$  of the constant current sink when  $R_3 \neq 0$ ? Express  $V_{o,min}$  as a function of  $I_o$ , which is the IC of Q1.

7. assuming  $R_3 \neq 0$   
 $\rightarrow$  consider voltage drop across resistor  $\{ V_{R_3} = I_e R_3$   
 $V_{o,min} = V_{EE} + 0.3V + I_e R_3$   
 now in terms of  $I_o$ :  $V_{o,min} = V_{EE} + 0.3V + [I_o (1 + 1/\beta)] R_3$

**Q8. (15 Points)** For  $V_{EE} = -5V$ , if we want to design a current sink with  $I_o = 1.0 \text{ mA}$  and  $V_{o,min} = -1.5 \text{ V}$  using the NPN-BJT 2N3094 characterized in Q1, what is the resistance value for  $R_3$ ? To reduce the DC power consumption of  $R_1$  and  $R_2$ , we usually choose large resistance values (in tens or hundreds of  $k\Omega$ ) for  $R_1$  and  $R_2$ . Suppose we choose  $R_2 = 100 \text{ k}\Omega$ , calculate  $R_1$  in  $k\Omega$ . Verify the  $I_o$  vs.  $V_{CC}$  characteristics of the design by sweeping  $V_{CC}$  from  $-5V$  to  $5V$  with a  $0.05V$  step and post the waveform of the simulated  $I_o$  vs.  $V_{CC}$  characteristics using the command "Window  $\rightarrow$  Copy to Clipboard" in the PSpice simulator window.

8.  $V_{EE} = -5V$   $V_{o,min} = V_{EE} + I_o R_3 + 0.3$   
 $I_o = 1.0 \text{ mA} = I_e$   
 $V_{o,min} = -1.5V$   $R_3 = \frac{V_{o,min} - V_{EE} - 0.3}{I_e}$   
 $R_2 = 100 \text{ k}\Omega$   
 $R_1 = ?$ ,  $R_3 = ?$   
 $I_c = I_o (1 + 1/\beta)$   $R_3 = \frac{V_{o,min} - V_{EE} - 0.3}{I_c (1 + 1/\beta)}$   
 $\beta = 117$   
 $V_{BE(on)} = 0.621V$   
 $\rightarrow$  From part 1  $R_3 = \frac{(-1.5) - (-5) - 0.3}{1 (1 + 1/117)} \approx R_3 = 3.17 \text{ k}\Omega$   
 given  $V_{BE} = \frac{R_1}{R_1 + R_2} V_{EE}$  First find  $V_B$ :  $V_B - V_{BE(on)} - I_e R_3 - V_{EE} = 0$   
 and  $R_{eq} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$   $V_B = V_{BE(on)} + I_e R_3 + V_{EE}$   
 $V_B = 0.621 + (1 + 1/117)(3.17) - 5 = -1.18V$   
 now  $V_{BE} - I_e R_{eq} = V_B$   
 $(-5) \left( \frac{R_1}{R_1 + 100} \right) - \left( \frac{I_o}{\beta} \right) \left( \frac{R_1 R_2}{R_1 + R_2} \right) = V_B \rightarrow \left( \frac{R_1}{(-5)(R_1 + 100)} \right) - \left( \frac{1}{117} \right) \left( \frac{100 R_1}{R_1 + 100} \right) = -1.18$   
 $\therefore R_1 = 25.3 \text{ k}\Omega$

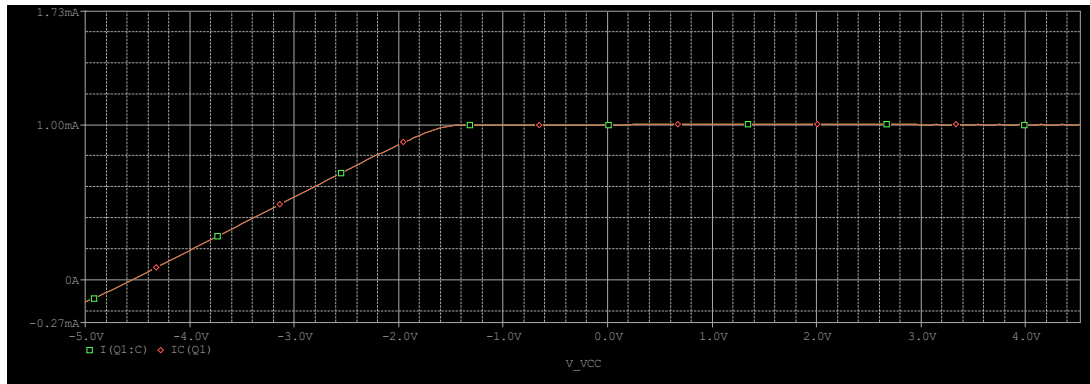


Figure 1: Plot of  $I_o$  VS  $V_{CC}$

**Q9. (10 Points)** When designing the constant current sink shown in Fig. 6, we assume that  $|V_{CE}| \geq 0.3V$  and Q1 works in the active region. Based on the resistance values obtained in Q8, sweep  $V_{CC}$  in Fig. 6 from -5 V to +5 V with a 0.05 V step and measure  $V_E$  and  $I_C$  to determine the  $|V_{CE}|$  required for Q1 to work in the active region.

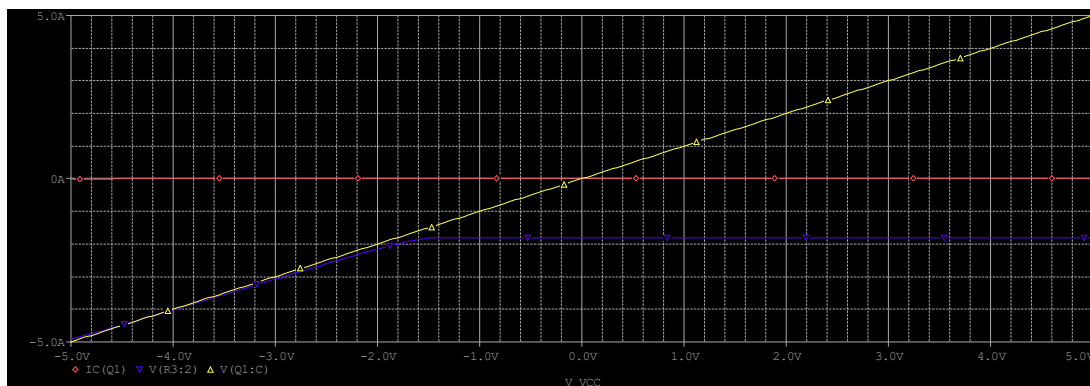


Figure 2: Plot of  $I_c$  VS  $V_E$  VS  $V_{CC}$

From the graph, we can see that  $V_E = -1.72 V$  and  $V_{CC} = -1.34 V$ . From this, we can calculate  $|V_{CE}|$  to be  $V_E - V_{CC} = -1.72 V + 1.34 V = 0.38 V$  which verifies the condition that  $|V_{CE}| \geq 0.3V$ .